



# St. Michael Polytechnic College

St. Santhiyagappar Nagar  
Kalayarkoil-630 551.



DEPT: EEE

YEAR/SEMESTER: II / III


SUB.NAME: Electrical Circuit Theory

## PART A

1. Define energy and give the expression.
2. State ohm's law.
3. Define resistance.
4. Define temperature coefficient of resistance.
5. Write the formula for equivalent resistance of three resistors connected in series.
6. Define electric field intensity.
7. Define current and mention its unit.
8. Write the relationship between voltage, charge and capacitance.
9. Write the formula for energy stored in a capacitor.
10. Write the formula for capacitance of parallel plate capacitor.

## PART B

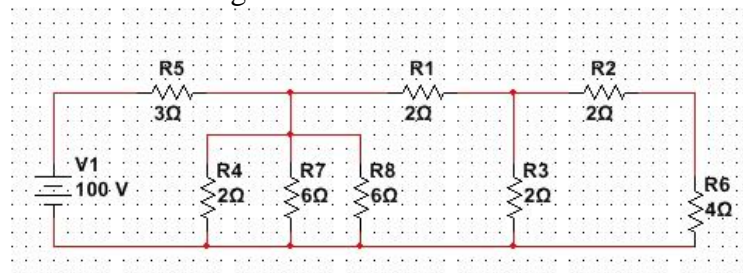1. Determine the current I for the given circuit.



2. A wheatstone bridge consists of  $AB \& BC = 10 \text{ ohm}$ ,  $CD = 4 \text{ ohm}$ ,  $DA = 5 \text{ ohm}$ . A galvanometer of  $20 \text{ ohm}$  resistance is connected across  $BD$ . Calculate the current through the galvanometer when a p.d. of  $10 \text{ volt}$  is maintained across  $A.C$ .
3. The total capacitance of two capacitors is  $0.333 \text{ F}$  when joined in series and  $1.5 \text{ F}$  when connected in parallel. Find the capacitance of each capacitor.